

# CAT 1: Transient Analysis of RL, RC, and RLC Circuits

David Muigai

March 27, 2025

## Question 1

### (a) Writing the Differential Equation

Using Kirchhoff's Voltage Law (KVL):

$$V = iR + L \frac{di}{dt} \quad (1)$$

$$24 = 10i + 2 \frac{di}{dt} \quad (2)$$

Rearranging to standard form:

$$2 \frac{di}{dt} + 10i = 24 \quad (3)$$

$$\frac{di}{dt} + 5i = 12 \quad (4)$$

This is our governing first-order differential equation.

### (b) Finding the Current $i(t)$ for $t > 0$

The general solution form for this type of equation is:

$$i(t) = A(1 - e^{-t/\tau}) \quad (5)$$

where  $\tau = \frac{L}{R}$  is the time constant.

At steady state ( $t = \infty$ ):

$$i = \frac{V}{R} = \frac{24}{10} = 2.4A \quad (6)$$

Therefore,  $A = 2.4$ .

The complete solution is:

$$i(t) = 2.4(1 - e^{-5t}) \quad \text{amperes, for } t > 0 \quad (7)$$

### (c) Calculations

Time constant:

$$\tau = \frac{L}{R} = \frac{2}{10} = 0.2 \text{ seconds} \quad (8)$$

To find  $i(0.5s)$ :

$$i(0.5) = 2.4(1 - e^{-5(0.5)}) \quad (9)$$

$$i(0.5) = 2.4(1 - e^{-2.5}) \quad (10)$$

$$i(0.5) = 2.4(1 - 0.082) \quad (11)$$

$$i(0.5) = 2.4(0.918) \quad (12)$$

$$i(0.5) = 2.20A \quad (13)$$

## Question 2

### (a) Deriving the Equation for Capacitor Charging

Using Kirchhoff's Voltage Law (KVL):

$$V = iR + v_c \quad (14)$$

where  $V = 20V$  (DC supply).

The current through the capacitor is:

$$i = C \frac{dv_c}{dt} \quad (15)$$

Substituting this into KVL:

$$20 = RC \frac{dv_c}{dt} + v_c \quad (16)$$

Rearranging to standard form:

$$RC \frac{dv_c}{dt} + v_c = 20 \quad (17)$$

Substituting given values:

$$(1000)(100 \times 10^{-6}) \frac{dv_c}{dt} + v_c = 20 \quad (18)$$

$$0.1 \frac{dv_c}{dt} + v_c = 20 \quad (19)$$

### (b) Solving for $v_c(t)$

This is a first-order differential equation with the general solution:

$$v_c(t) = A(1 - e^{-t/\tau}) \quad (20)$$

where  $\tau = RC$  is the time constant.

At  $t = \infty$ ,  $v_c = 20V$  (capacitor fully charged), so  $A = 20$ .

Thus, the complete solution is:

$$v_c(t) = 20(1 - e^{-t/0.1}) \text{ volts, for } t > 0 \quad (21)$$

### (c) Calculations

Time constant:

$$\tau = RC = (1000)(100 \times 10^{-6}) = 0.1 \text{ seconds} = 100 \text{ ms} \quad (22)$$

To find  $v_c(10\text{ms})$ :

$$v_c(10\text{ms}) = 20(1 - e^{-0.01/0.1}) \quad (23)$$

$$v_c(10\text{ms}) = 20(1 - e^{-0.1}) \quad (24)$$

$$v_c(10\text{ms}) = 20(1 - 0.905) \quad (25)$$

$$v_c(10\text{ms}) = 20(0.095) \quad (26)$$

$$v_c(10\text{ms}) = 1.9\text{V} \quad (27)$$

## Question 3

### (a) Deriving the Equation for Current Decay

After disconnection, using KVL:

$$0 = iR + L \frac{di}{dt} \quad (28)$$

where  $i$  = current,  $R = 15\Omega$ ,  $L = 3H$ .

Rearranging:

$$L \frac{di}{dt} = -iR \quad (29)$$

$$3 \frac{di}{dt} = -15i \quad (30)$$

$$\frac{di}{dt} = -5i \quad (31)$$

This is our governing differential equation for current decay.

### (b) Finding $i(t)$ after Disconnection

For a decaying current, the solution form is:

$$i(t) = Ae^{-t/\tau} \quad (32)$$

where  $\tau = \frac{L}{R} = \frac{3}{15} = 0.2$  seconds.

At  $t = 0$ ,  $i = 5\text{A}$  (initial current).

Therefore,

$$5 = A \quad (33)$$

The complete solution is:

$$i(t) = 5e^{-5t} \text{ amperes} \quad (34)$$

**(c) Calculating Current at  $t = 1s$**

$$i(1) = 5e^{-5(1)} \quad (35)$$

$$i(1) = 5e^{-5} \quad (36)$$

$$i(1) = 5(0.0067) \quad (37)$$

$$i(1) = 0.0335A \approx 33.5mA \quad (38)$$

## **Question 4. Solving the RLC Circuit Problem Step by Step**

### **(a) Writing the Second-Order Differential Equation**

For a series RLC circuit with a DC voltage source  $V$ , using Kirchhoff's Voltage Law:

$$V = L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt \quad (39)$$

Taking the derivative of both sides to eliminate the integral:

$$0 = L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i \quad (40)$$

Therefore, the governing differential equation is:

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0 \quad (41)$$

Substituting the given values:

$$(1) \frac{d^2i}{dt^2} + (50) \frac{di}{dt} + \left( \frac{1}{100 \times 10^{-6}} \right) i = 0 \quad (42)$$

$$\frac{d^2i}{dt^2} + 50 \frac{di}{dt} + 10^4 i = 0 \quad (43)$$

### **(b) Identifying the Damping Type**

Calculate the damping coefficient ( $\alpha$ ) and natural frequency ( $\omega_0$ ):

$$\alpha = \frac{R}{2L} = \frac{50}{2 \times 1} = 25 \quad (44)$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{1 \times 100 \times 10^{-6}}} = 100 \quad (45)$$

Calculate the discriminant ( $\alpha - \omega_0$ ):

$$25 - 100 = -75 \quad (46)$$

Since  $\alpha < \omega_0$ , this is an underdamped system. The general solution form is:

$$i(t) = e^{-\alpha t} [A \cos(\omega_d t) + B \sin(\omega_d t)] \quad (47)$$

where:

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{9375} \approx 96.8 \text{ rad/s} \quad (48)$$

$$i(t) = Ae^{-25t} [\cos(96.8t) + B \sin(96.8t)] \quad (49)$$

### (c) Natural Frequencies and Behavior

Damped natural frequency:

$$\omega_d \approx 96.8 \text{ rad/s} \quad (50)$$

Undamped natural frequency:

$$\omega_0 = 100 \text{ rad/s} \quad (51)$$

The circuit behavior over time:

- The current will oscillate with frequency  $\omega_d \approx 96.8 \text{ rad/s}$ .
- The amplitude will decay exponentially with time constant  $\tau = \frac{1}{\alpha} = \frac{1}{25} = 0.04 \text{ seconds}$ .
- Since it's underdamped, the current will oscillate around zero while gradually decreasing in amplitude.
- The system will eventually settle to zero current ( $t \rightarrow \infty$ ) since there's only a DC source and the circuit is initially unenergized.
- The response will effectively reach steady state after approximately  $5\tau = 0.2 \text{ seconds}$ .

## Question 5. Deriving the Characteristic Equation

### (a) Writing the Second-Order Differential Equation

For a series RLC circuit with a step voltage input  $V(t)$ , using Kirchhoff's Voltage Law:

$$V(t) = L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt \quad (52)$$

Taking the derivative to eliminate the integral:

$$0 = L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i \quad (53)$$

Substituting the given values:

$$0.5 \frac{d^2i}{dt^2} + 5 \frac{di}{dt} + \left( \frac{1}{50 \times 10^{-6}} \right) i = 0 \quad (54)$$

Simplifying:

$$\frac{d^2i}{dt^2} + 10 \frac{di}{dt} + 40000i = 0 \quad (55)$$

The characteristic equation is:

$$s^2 + 10s + 40000 = 0 \quad (56)$$

### (b) Testing for Underdamped Condition and Finding Damped Frequency

Calculate the damping coefficient ( $\alpha$ ) and natural frequency ( $\omega_0$ ):

$$\alpha = \frac{R}{2L} = \frac{5}{2 \times 0.5} = 5 \quad (57)$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{0.5 \times 50 \times 10^{-6}}} = 200 \text{ rad/s} \quad (58)$$

For the underdamped condition:  $\alpha < \omega_0$

$$5 < 200, \quad \text{therefore the system is underdamped} \quad (59)$$

Damped frequency:

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad (60)$$

$$\omega_d = \sqrt{40000 - 25} \quad (61)$$

$$\omega_d = \sqrt{39975} \approx 199.94 \text{ rad/s} \quad (62)$$

### (c) Time for Oscillations to Decay to 10%

For an underdamped system, the envelope of decay is  $e^{-\alpha t}$ . We want to find  $t$  when amplitude reaches 10% of initial:

$$0.1 = e^{-5t} \quad (63)$$

Taking the natural logarithm:

$$\ln(0.1) = -5t \quad (64)$$

$$t = \frac{-\ln(0.1)}{5} \quad (65)$$

$$t \approx 0.46 \text{ seconds} \quad (66)$$

Therefore, it takes approximately 0.46 seconds for the oscillations to decay to 10% of their initial amplitude.

The complete solution can be written as:

$$i(t) = Ae^{-5t} [\cos(199.94t) + B \sin(199.94t)] \quad (67)$$

where  $A$  and  $B$  are constants determined by initial conditions.