



CHUKA UNIVERSITY

FACULTY OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

EENG 465 Power Systems II

CAT 1

Group Members

Johnson Kiama	EB24/56163/21
Mary Wangari	EB24/56151/21
David Muigai	EB24/56171/21
Johnson Munyasia	EB24/56157/21
Elijah Karanja	EB24/56201/21

Question 1

A 275 kV overhead transmission line has the following characteristics: $Z = 12.5 + j66 \Omega$, $Y = j4.4 \times 10^{-4} S$ The line delivers 250 MW at a lagging power factor of 0.9. Determine:

- (i) ABCD constants
- (ii) Surge impedance of the line
- (iii) Sending-end voltage
- (iv) Sending-end current
- (v) Line charging current
- (vi) Transmission efficiency
- (vii) Voltage regulation

Solution

Given:

$$\begin{aligned} Z &= 12.5 + j66, \quad Y = 4.4 \times 10^{-4} \angle 90^\circ \\ P &= 250 \text{ MW}, \quad V_R = 275 \text{ kV}, \quad \cos \phi_R = 0.9 \\ \phi_R &= \cos^{-1} 0.9 = 25.842^\circ \end{aligned}$$

The receiving end active power is given by ,

$$P = \sqrt{3} V_R I_R \cos \phi_R \quad (1)$$

$$I_R = \frac{250 \times 10^6}{\sqrt{3} \times 275 \times 10^3 \times 0.9} = 583.18 \text{ A} \quad (2)$$

$$I_R = 583.18 \angle -25.842^\circ \text{ A}$$

(i) Calculating ABCD constant for long transmission line,

$$A = D = \cosh \gamma = \frac{1}{2} [e^{\alpha + j\beta} + e^{-(\alpha + j\beta)}] \quad (3)$$

$$A = D = \frac{1}{2} [e^{\alpha \angle \beta} + e^{-\alpha \angle -\beta}]$$

$$\gamma = \sqrt{ZY} \quad (4)$$

$$\gamma = \sqrt{(12.5 + j66) \times (4.4 \times 10^{-4} \angle 90^\circ)}$$

$$\gamma = \sqrt{0.0295 \angle 169.27^\circ}$$

$$\gamma = 0.172 \angle 84.635^\circ = 0.0160 + j0.171 \quad (5)$$

comparing with $\alpha + j\beta$, we get the following

$$\alpha = 0.0160 \text{ rad}, \quad \beta = \frac{0.171 \times 180}{\pi} = 9.797^\circ$$

$$A = D = \frac{1}{2} [e^{0.016 \angle 9.797^\circ} + e^{-0.016 \angle -9.797^\circ}] \quad (6)$$

$$A = D = 0.9855 \angle 0.1582^\circ \quad (7)$$

$$\sinh \gamma = \frac{1}{2} [e^{\alpha \angle \beta} - e^{-\alpha \angle -\beta}] \quad (8)$$

$$= \frac{1}{2} [e^{0.016 \angle 9.797^\circ} - e^{-0.016 \angle -9.797^\circ}]$$

$$\sinh \gamma = 0.171 \angle 84.71^\circ \quad (9)$$

(ii) The surge impedance of the line (Z_0) is given as,

$$Z_0 = \sqrt{\frac{Z}{Y}} \quad (10)$$

Substituting the given values:

$$Z_0 = \sqrt{\frac{12.5 + j66}{j4.4 \times 10^{-4}}}$$

$$Z_0 = \sqrt{152666.55 \angle -10.724^\circ}$$

$$Z_0 = 390.725 \angle -5.362^\circ \Omega \quad (11)$$

so that

$$B = Z_0 \sinh \gamma \quad (12)$$

$$B = 390.725 \angle -5.362^\circ \times 0.171 \angle 84.71^\circ$$

$$B = 66.814 \angle 79.348^\circ \quad (13)$$

$$C = \frac{\sinh \gamma}{Z_0} = \frac{0.171 \angle 84.71^\circ}{390.725 \angle -5.36^\circ} \quad (14)$$

$$C = 4.376 \times 10^{-4} \angle 90.072^\circ \quad (15)$$

(iii) Sending end voltage is given as,

$$V_s = AV_R + BI_R \quad (16)$$

$$V_s = (0.9855 \angle 0.1582^\circ) \times \left(\frac{275 \times 10^3}{\sqrt{3}} \right) \\ + (66.814 \angle 79.348^\circ) \times (583.18 \angle -25.842^\circ)$$

$$V_s = 182427.57 \angle 0.025^\circ V \quad (17)$$

(iv) Sending end current is given as,

$$I_s = CV_R + DI_R \quad (18)$$

$$I_s = \left(4.376 \times 10^{-4} \angle 90.072^\circ \right) \left(\frac{275 \times 10^3}{\sqrt{3}} \angle 0^\circ \right) \\ + (0.9855 \angle 0.1582^\circ) (583.18 \angle -25.842^\circ)$$

$$I_s = 69.478 \angle 90.072^\circ + 574.72 \angle -25.68^\circ \\ I_s = 548.12 \angle -19.12^\circ A \quad (19)$$

(v) The line charging current is given by:

$$I_c = j\omega CV_R \quad (20)$$

From the ABCD calculations:

$$C = 4.376 \times 10^{-4} \angle 90.072^\circ$$

$$I_c = \left(4.376 \times 10^{-4} \angle 90.072^\circ \right) \times \left(\frac{275 \times 10^3}{\sqrt{3}} \right)$$

$$I_c = 69.478 \angle 90.072^\circ A \quad (21)$$

Sending end power factor,

$$\phi_s = 0.025^\circ - (-19.12^\circ) = 19.145^\circ \quad (22)$$

$$\cos \phi_s = \cos 19.145^\circ = 0.9448 \quad (23)$$

(vi) Calculating the transmission efficiency of the line,

$$\eta = \frac{\text{Output}}{\text{Input}} = \frac{3V_R I_R \cos \phi_R}{3V_S I_S \cos \phi_S} \quad (24)$$

$$\eta = \frac{250 \times 10^6}{3 \times 182427.57 \times 548.12 \times 0.8733}$$

$$\eta = 95.43\% \quad (25)$$

(vii) Finally the Voltage regulation of transmission line,

$$\text{Regulation} = \frac{\left| \frac{V_S}{A} \right| - |V_R|}{|V_R|} \quad (26)$$

$$= \frac{\frac{182427.57}{0.9855} - \frac{275 \times 10^3}{\sqrt{3}}}{\frac{275 \times 10^3}{\sqrt{3}}}$$

$$= 0.1659 = 16.59\% \quad (27)$$

2. (15 pts.) Consider the following system:

[Diagram not shown]

Here, the system F is defined by the input-output relationship

$$F\{z[n]\} = z[n] - z[n-1],$$

and Δ is the unit delay

$$\Delta\{w[n]\} = w[n-1].$$

Write down the linear difference equation describing this system.

Solution. Let $z[n]$ be the output of the summer, as shown above. Then

$$y[n] = F\{z[n]\} = z[n] - z[n-1].$$

Now,

$$z[n] = 2x[n] - \Delta\{y[n]\} = 2x[n] - y[n-1].$$

Therefore, substituting the expression for $z[n]$ into the first equation, we can write

$$\begin{aligned} y[n] &= z[n] - z[n-1] \\ &= \underbrace{2x[n] - y[n-1]}_{=z[n]} - \underbrace{2x[n-1] - y[n-2]}_{=z[n-1]} \\ &= 2x[n] - y[n-1] - 2x[n-1] + y[n-2]. \end{aligned}$$

$$\boxed{y[n] + y[n-1] - y[n-2] = 2x[n] - 2x[n-1]}$$